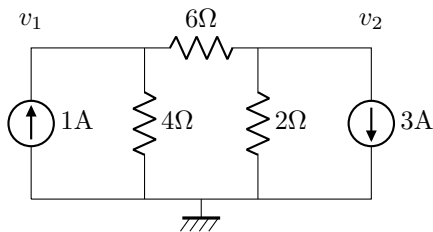


Lecture 12, Feb 7, 2022

Nodal Analysis

- Nodal analysis is an algorithmic method for circuit analysis; it finds the node voltages at every node in the circuit
 - Define *node voltage* as the voltage between a node and a reference point (common ground), with positive polarity at the node and negative polarity at the reference point
 - The reference (ground) node is typically denoted with a ground symbol: \perp or ////
- Apply KCL for every node in terms of the node voltages
 - Voltage between two nodes is the difference of their nodal voltages
 - $v_{AB} = v_A - v_B$ and $v_{BA} = v_B - v_A$
- Procedure:
 1. Find all the nodes in the circuit and label them, choose one as ground
 - Choice of ground node is arbitrary but sometimes it can simplify the math
 - Choose the node that's connected to the highest number of voltage sources; prefer independent sources over dependent sources
 2. Assume current directions/signs (negative for current entering node, positive for current leaving)
 3. Write KCL for all the ungrounded nodes
 - Current sources: we have voltage directly, resistors: use Ohm's law
 - If we have a voltage source between the ground node and another node, we can get the voltage of that node directly
 - Usually we always write the current that leaves a node via a resistor since it gives a positive sign
 4. Solve the system for the nodal voltages and use the nodal voltages to find anything else needed
- Example circuit 1:




– KCL at node 1: $-1 + \frac{v_1 - 0}{4} + \frac{v_1 - v_2}{6} = 0$

* KCL at node 2: $3 + \frac{v_2 - 0}{2} + \frac{v_2 - v_1}{6} = 0$

* Solution: $v_1 = \frac{2}{3}\text{V}, v_2 = -\frac{13}{2}\text{V}$

- Example circuit 2:

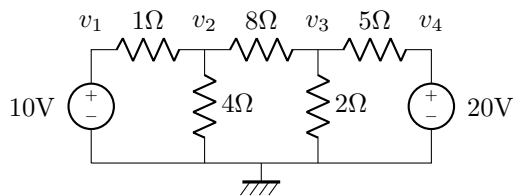

– We get $v_1 = 10\text{V}, v_2 = 20\text{V}$ immediately

* Node 2: $\frac{v_2 - v_1}{1} + \frac{v_2 - 0}{4} + \frac{v_2 - v_3}{8} = 0$

* Node 3: $\frac{v_3 - v_2}{8} + \frac{v_3 - 0}{2} + \frac{v_3 - v_4}{5} = 0$

* Solution: $v_2 = 7.82\text{V}, v_3 = 6.03\text{V}$